

Assignment 6

mahesh

January 2, 2021

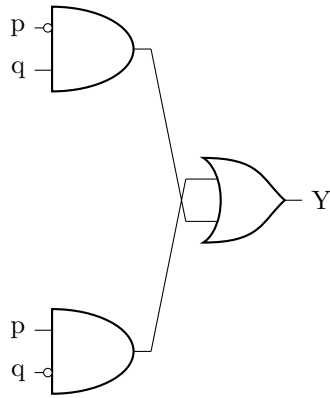


Figure 1: Logic Gate

$$Y = p \cdot \bar{q} + q \cdot \bar{p} \quad (1)$$