

Assignment 7

mahesh

January 3, 2021

1 question

The expression $\sim (p \leftrightarrow q)$ is equivalent to:

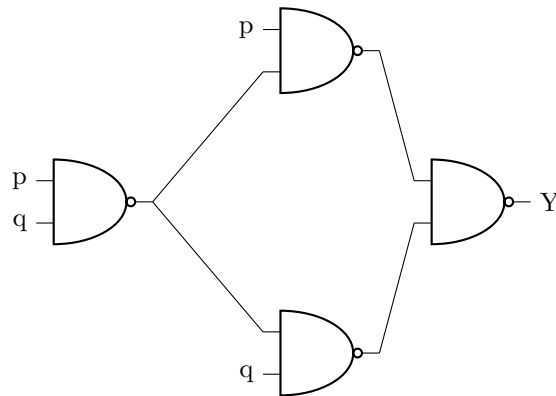


Figure 1: Logic Gate for NAND logic

$$Y = p.\bar{q} + q.\bar{p} \quad (1)$$